

**Final exam DITE:** Tuesday, January 14, 2014 -- 14:00 to 17:00h

**Task I:** Design two versions (**Version A** and **Version B** below) of the combinational circuit whose input is a 4-bit number and whose output is the 2's complement of the input number:

**Version A)** – The circuit is a simplified two-level circuit, plus inverters as needed for the input variables.

**Version B)** – The circuit is made up of four identical two-input, two-output cells, one for each bit. The cells are connected in cascade, with lines similar to a carry between them. The value applied to the rightmost carry bit is 0.

**Important:** Show and explain all the steps you do to implement the circuit above.

**Task II:** Implement one SR flip-flop using the following components: one T flip-flop and one Multiplexer 4-to-1.

**Important:** Show and explain all the steps you do to implement the circuit above.

**Task III:** A sequential circuit with two flip-flops A and B, one input X, and one output Z is specified by the following equations:

$$A(t+1) = X(t)'A(t) + X(t)B(t)$$

$$B(t+1) = X(t)'A(t)'$$

$$Z(t) = X(t)A(t) + X(t)'B(t)'$$

Transform and implement the circuit described above as **Moore Finite State**

**Machine (FSM)** under the following conditions:

1. Use **only** NOR gates and JK Flip-Flops;
2. Derive and show the state table of the Moore FSM;
3. Derive and show the state diagram of the Moore FSM;
4. Draw the logic diagram of the Moore FSM.

**Important:** Show and explain all the steps you do to implement the circuit above.