

**Midterm exam DITE:** Wednesday, October 25, 2017 -- 10:00 to 13:00h

**Task I (6 points):** Simplify the Boolean function  $F(W,X,Y,Z) = \sum m(1,2,4,5,6,8,9)$  which has the don't-care conditions  $d(W,X,Y,Z) = \sum m(10,11,14,15)$  by finding all prime implicants and essential prime implicants and applying the selection rule. Note that function  $F$  has *don't care* conditions  $d$  that you have to take into account when simplifying function  $F$ . After you have simplified the function, represent it using the logic basis NAND. Also, draw the combinational logic circuit corresponding to the function using only NAND gates.

**Note:** Show all prime implicants and essential prime implicants

**Task II (4 points):** A combinational circuit is defined by the following three Boolean functions:

$$F1 = (X+Z)' + XYZ$$

$$F2 = X'Z' + X'YZ$$

$$F3 = XY'Z + (X+Z)'$$

Design the circuit with a single 4-to-1\_3-line Multiplexer and one XOR gate.

**Task III (4 points):** A combinational circuit is defined by the following two Boolean functions:

$$A1 = (X'+Z) + XYZ$$

$$A2 = (X+Z)' + X'YZ$$

Design the circuit with a single 3-to-8 Decoder and external NOR gates.

**Task IV (6 points):** Design a combinational logic circuit with 4 inputs that generates a 1 when the number of 0s on the inputs equals the number of 1s or the number of 0s on the inputs equals to 1. Use only 2-input NOR gates to implement the circuit.

**Note:** During the design you must simplify the circuit using K-map

**Important:** For all four tasks above do not forget to show how you obtained the results, step by step!

**The exam grade is equal to the obtained number of points divided by 2!**